

Problem 7 (Purcell 9.13)

parallel:

$$E_{\parallel}^2 - B_{\parallel}^2 = \vec{E}_{\parallel} \cdot \vec{E}_{\parallel} - \vec{B}_{\parallel} \cdot \vec{B}_{\parallel} = \vec{E}_{\parallel} \cdot \vec{E}_{\parallel} - \vec{B}_{\parallel} \cdot \vec{B}_{\parallel}$$


perpendicular:

$$\begin{aligned} E_{\perp} \cdot E_{\perp} - B_{\perp} \cdot B_{\perp} &= \gamma^2 (\vec{E}_{\perp} + \vec{\beta} \times \vec{B}_{\perp}) \cdot (\vec{E}_{\perp} + \vec{\beta} \times \vec{B}_{\perp}) \\ &\quad - \gamma^2 (\vec{B}_{\perp} - \vec{\beta} \times \vec{E}_{\perp}) \cdot (\vec{B}_{\perp} - \vec{\beta} \times \vec{E}_{\perp}) \\ &= \gamma^2 (E_{\perp}^2 (1 - \beta^2) - B_{\perp}^2 (1 - \beta^2)) = E_{\perp}^2 - B_{\perp}^2 \end{aligned}$$

$$E^2 - B^2 = E_{\parallel}^2 - B_{\parallel}^2 + E_{\perp}^2 - B_{\perp}^2 = E^2 - B^2$$

HOMEWORK #9

Problem 1 (Purcell 7.13)

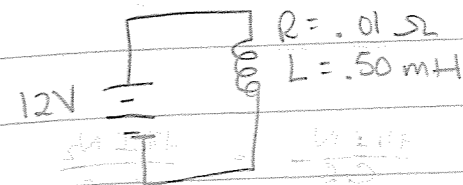

current: $I = I_0 (1 - \exp(-\frac{Rt}{L}))$

$$.9 = 1 - e^{-Rt/L}$$

$$t_0 = .115 \text{ s}$$


energy stored in magnetic field:

$$U = \frac{1}{2} L I^2 = \frac{1}{2} (.5 \times 10^{-3}) (.9 \times \frac{12}{0.01})^2 = \frac{1}{2} (.5 \times 10^{-3}) (1080)^2 = 292 \text{ J}$$

energy withdrawn from battery:

$$\begin{aligned} U &= \int \mathcal{E} I dt \\ &= \mathcal{E} \int_0^{t_0} (1 - e^{-Rt/L}) dt \\ &= 1008 \text{ J} \end{aligned}$$

7.14

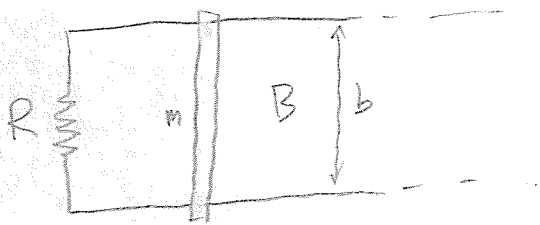

$$a) \quad \mathcal{E} = -\frac{1}{c} \frac{d\Phi}{dt} = -\frac{1}{c} \frac{d}{dt} (B l v) = -\frac{B l v}{c}$$

$$\Rightarrow I = \frac{\mathcal{E}}{R} = -\frac{B l v}{c R}$$

$$\Rightarrow \vec{F} = \frac{I \vec{l} \times \vec{B}}{c} = -\frac{I B l}{c} \hat{x}$$

$$\Rightarrow a = \frac{|\vec{F}|}{m} = -\frac{I B l}{c m} = -\frac{b^2 B^2 v}{c^2 R m} = \frac{dv}{dt}$$

$$\Rightarrow v = v_0 e^{-\frac{b^2 B^2 t}{c^2 R m}}$$

$v \rightarrow 0$ as $t \rightarrow \infty$ but v is never 0.

$$b) \quad x = \int_0^{\infty} v(t) dt = \int_0^{\infty} v_0 e^{-\frac{b^2 B^2 t}{c^2 R m}} dt = -\frac{v_0 c^2 R m}{b^2 B} e^{-\frac{b^2 B^2 t}{c^2 R m}} \Big|_0^{\infty}$$

$$= \boxed{\frac{v_0 c^2 R m}{b^2 B}}$$

$$c) \quad \frac{1}{2} m v_0^2 = \int_0^{\infty} I^2 R dt$$

$$= \int_0^{\infty} \left(\frac{B l v}{c R} \right)^2 R dt = \frac{B^2 l^2}{c^2 R} \int_0^{\infty} v^2 dt$$

$$= \frac{B^2 l^2}{c^2 R} \int_0^{\infty} v_0^2 e^{-\frac{2 b^2 B^2 t}{c^2 R m}} dt = \frac{B^2 l^2}{c^2 R} \left(v_0^2 \frac{c^2 R m}{2 b^2 B^2} \right)$$

$$= \frac{1}{2} m v_0^2 \quad \checkmark$$

8.2 $R = 2000 \Omega$ $120V$ rms
 $C = 1 \mu F$ $60 Hz$

a) Impedance = Z

$$Z = R - \frac{j}{\omega C} = 2000 \Omega - \frac{j}{60 Hz \cdot 1 \mu F} = \boxed{(2000 - 1.6 \times 10^4 j) \Omega}$$

b) RMS value of current

$$I_{rms} = \sqrt{|Y V|^2}$$

$$= V_{rms} \left(\left(\frac{1}{R} \right)^2 + (\omega C)^2 \right)^{\frac{1}{2}}$$

$$= 120V \left(\left(\frac{1}{2000 \Omega} \right)^2 + (60 Hz \cdot 10^{-6} F)^2 \right)^{\frac{1}{2}}$$

$$= \boxed{0.0604 A}$$


c) $\bar{P} = \frac{V_{rms}^2}{R} = \frac{(120V)^2}{2000 \Omega} = \boxed{7.2 W}$

d) $V_C = \frac{V_{rms}}{R - \frac{j}{\omega C}} \left(-\frac{j}{\omega C} \right) = \frac{120V}{(2000 - 1.6 \times 10^4 j) \Omega} \left(-\frac{j}{60 Hz \cdot 10^{-6} F} \right)$

$$= \boxed{(418.758 - 14.3 j) V}$$

$$V_R = 120 - V_C = \boxed{(1.242 + 14.3 j) V}$$

e)

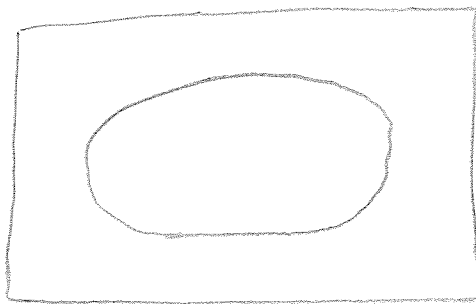

← An oval

Problem 3 (Purcell 7.21)

$\epsilon_0 = \frac{1}{4\pi k c^2}$ } for unit conversions
 $\epsilon_0 \mu_0 = \frac{1}{c^2}$

field inside a solenoid: $\frac{4\pi I N}{c l} = \frac{4\pi I N_2}{b_2 c}$

inductance $\epsilon_{21} = M_{21} \frac{dI}{dt}$

$M_{21} = \frac{\Phi}{I} = \frac{4\pi \mu_0}{b_2 c^2} \pi a_1^2 N_1$

$\epsilon_{21} = \frac{4\pi^2 N_2 N_1 a_1^2}{b_2 c^2}$

Problem 5 (Purcell 8.3)



$R = 1000 \Omega$

$C = 500 \text{ pF}$

$L = 2 \text{ mH}$

$Z^{-1} = \left(\frac{1}{R} + \frac{1}{i\omega L} + \frac{\omega C}{-i} \right)$

$Z = \frac{1}{\left(\frac{1}{R} + \frac{1}{i\omega L} - \frac{\omega C}{i} \right)}$

a) $\omega = 10 \text{ Kilocycles/sec.} = 10,000 \text{ Hz}$

$Z = \frac{1}{\frac{1}{1000} + \frac{1}{i(10,000)(.002)} - \frac{(10,000)(5 \times 10^{-10})}{i}}$

$Z = \frac{1}{\frac{1}{1000} - i \left(\frac{1}{10000} \cdot \frac{1}{.002} \right) - i (10000 \times 5 \times 10^{-10})}$

$Z = \frac{1}{.001 - i (.05 + .000005)} = \frac{1}{.001 - i (.050005)}$

$Z = \frac{1}{.001 - i (.050005)} \cdot \frac{.001 + i (.050005)}{.001 + i (.050005)}$

$= \frac{.001 + i (.050005)}{1 \times 10^{-6} + .00250005} = .4 + 20i$

- $i^{-1} = -i$
- $i^0 = 1$
- $i = i$
- $i^2 = -1$

b) $\omega = 10^6 \text{ Hz}$

Complex Power

same method as in part a

$Z = 39.2 - 194.1i$

Hint 2

c) maximize Z with respect to ω

$$\frac{dZ}{d\omega} = -1 \left(\frac{1}{R} + \frac{1}{i} \left(\frac{1}{\omega L} - \omega C \right) \right)^2 \left[\frac{-\omega^{-2}}{iL} - \frac{C}{i} \right] = 0$$

$$\frac{1}{iL} \omega^{-2} - \frac{C}{i} = 0$$

$$\frac{1}{L} \omega^{-2} = \frac{C}{i}$$

$$\omega^{-2} = LC$$

$$\frac{1}{\omega^2} = LC$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \sqrt{\frac{1}{LC}}$$

↑
resonant frequency

8.4



Work out equation analogous to (8-2):

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = 0$$

$$\textcircled{1} I = -\frac{dQ}{dt} \quad \textcircled{2} Q = CV \quad \textcircled{3} V = I_1 R' = L \frac{dI_2}{dt} \quad \textcircled{4} I_1 + I_2 = I$$

$$\textcircled{4} I_1 + I_2 = I \stackrel{\textcircled{1}}{\Rightarrow} \frac{V}{R'} + I_2 \stackrel{\textcircled{2}}{=} -C \frac{dV}{dt}$$

$$\Rightarrow I_2 = -C \frac{dV}{dt} - \frac{V}{R'}$$

$$\stackrel{\textcircled{3}}{\Rightarrow} V = L \frac{d}{dt} \left(-C \frac{dV}{dt} - \frac{V}{R'} \right)$$

$$\Rightarrow V = -LC \frac{d^2V}{dt^2} - \frac{L}{R'} \frac{dV}{dt}$$

$$\Rightarrow \boxed{\frac{d^2V}{dt^2} + \frac{1}{R'C} \frac{dV}{dt} + \frac{V}{LC} = 0}$$

Using (8-3, 4, 5):

$$\Rightarrow (\alpha^2 - \omega^2) \cos \omega t + 2\alpha\omega \sin \omega t - \frac{1}{R'C} (\alpha \cos \omega t + \omega \sin \omega t) + \frac{1}{LC} (\cos \omega t) = 0$$

The coefficients of $\sin + \cos$ must each be zero:

$$\Rightarrow \alpha^2 - \omega^2 - \frac{\alpha}{R'C} + \frac{1}{LC} = 0 \quad \text{and} \quad 2\alpha\omega - \frac{\omega}{R'C} = 0$$

$$\Rightarrow \boxed{\alpha = \frac{1}{2R'C}} \quad \leftarrow$$

$$\Rightarrow \omega^2 = \alpha^2 - \frac{\alpha}{R'C} + \frac{1}{LC} = \frac{1}{4R'^2C^2} - \frac{1}{2R'C^2} + \frac{1}{LC}$$

$$\Rightarrow \boxed{\omega^2 = \frac{1}{LC} - \frac{1}{4(R'C)^2}}$$


To be the same as a series RLC

$$\frac{R}{L} = \frac{1}{R'C} \Rightarrow \boxed{R' = \frac{L}{RC}}$$

8.6

$$V(t) = Ae^{-\beta t}$$

By (8-2)

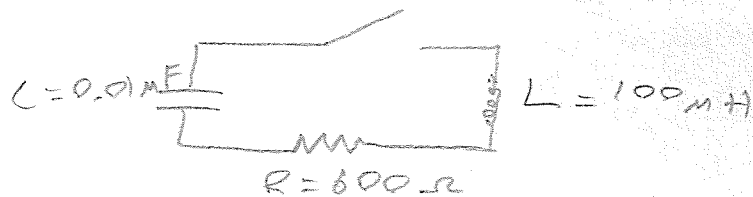

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

$$\Rightarrow (A\beta^2 e^{-\beta t}) + \frac{R}{L} (-\beta A e^{-\beta t}) + \frac{1}{LC} (A e^{-\beta t}) = 0$$

$$\Rightarrow \beta^2 - \frac{R}{L}\beta + \frac{1}{LC} = 0$$

$$\Rightarrow \beta = \frac{\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$= \frac{\frac{R}{L} \pm \frac{R}{L} \sqrt{1 - \frac{4L}{CR^2}}}{2}$$

$$= \frac{R}{2L} \left(1 \pm \sqrt{1 - \frac{4L}{CR^2}} \right)$$

$$= \boxed{\frac{5.82 \times 10^6 \text{ Hz}}{\beta_1} \quad \text{or} \quad \frac{1.72 \times 10^5 \text{ Hz}}{\beta_2}}$$

$$\Rightarrow V(t) = A e^{-\beta_1 t} + B e^{-\beta_2 t} \quad (8-16)$$

$$V(0) = A + B = V$$

$$\left. \frac{dV}{dt} \right|_{t=0} = 0 = -\beta_1 A - \beta_2 B$$

$$\Rightarrow \boxed{\frac{B}{A} = -\frac{\beta_1}{\beta_2} = -33.97}$$