

171.106: Electromagnetic Theory I

Midterm Exam 4/15/10 1:30-2:30

A letter sized paper with formulae on one side is permitted and check out the formula page as well. Start each problem on a fresh page and please give detailed reasoning. If in a later question you need a result from a question that you cannot solve then write formulae with the unknown as a symbol and you will get due credit. Ask your proctor for clarification if the text is unclear.

Problem 1 (30 points)

Consider Hall's experiment indicated in Fig. 1. The material is a metal with a density, n , of charge carriers each with charge, q and mass, m . The Hall voltage, V_H , is measured for a given applied field, B , current, I , and conductor thickness, t . From these numbers the so called Hall coefficient for the material is determined:

$$R_H = \frac{tV_H}{IB}.$$

- (a) Show that the Hall coefficient $R_H = \frac{1}{nqc}$ (CGS units)

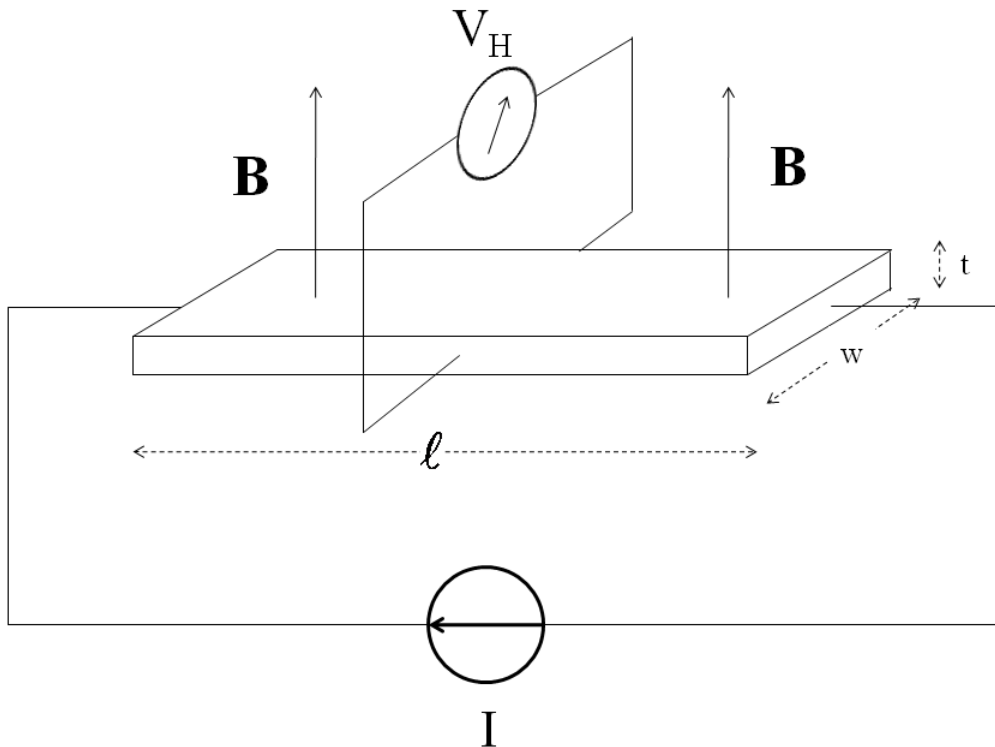


Figure 1.

Problem 2 (20 points)

In the following B is a constant with dimension of magnetic field and d is a constant of dimension length. $\mathbf{r} = x\hat{\mathbf{x}} + y\hat{\mathbf{y}} + z\hat{\mathbf{z}}$ is the position vector.

Which of the following could be expressions for a spatially varying magnetic field.

(a) $\mathbf{B}(\mathbf{r}) = \frac{B}{d}\mathbf{r}$

(b) $\mathbf{B}(\mathbf{r}) = \frac{B}{d}(x\hat{\mathbf{x}} + y\hat{\mathbf{y}} - 2z\hat{\mathbf{z}})$

Hint: There are no magnetic monopoles!

Problem 3 (25 points)

Consider the circuit shown in Fig. 2. Here we assume that the current source is providing a fixed current, I_s , and the battery has an EMF voltage \mathcal{E}_s .

- (a) Determine the current, I_2 , through the resistor.
- (b) Determine the total power dissipated in the circuit

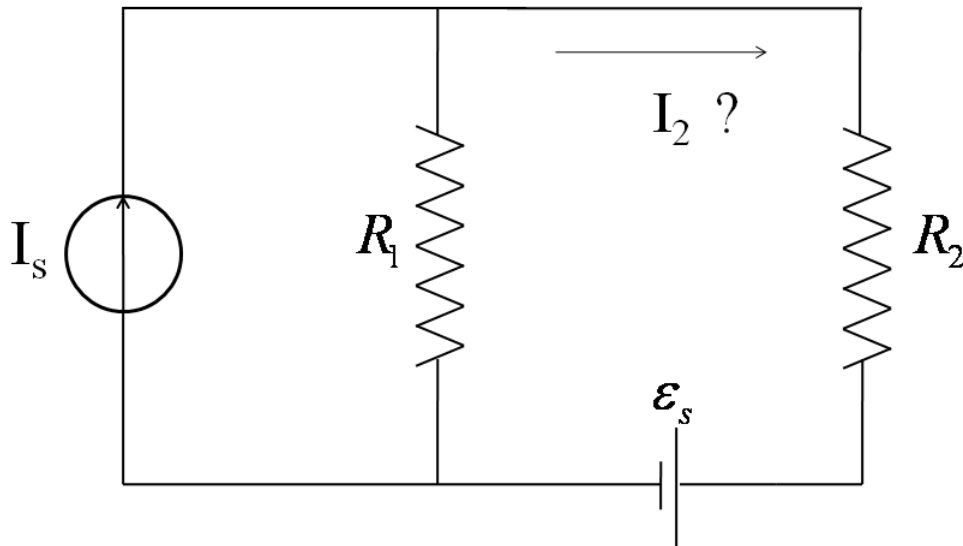


Figure 2.

Problem 4 (25 points)

Consider the circuit shown in Fig. 3. After a long period with the switch open (as shown), the switch is closed at time $t \equiv 0$.

- Determine an expression for the time dependent current through the inductor.
- Determine how much energy is dissipated in the resistor after the switch is closed.

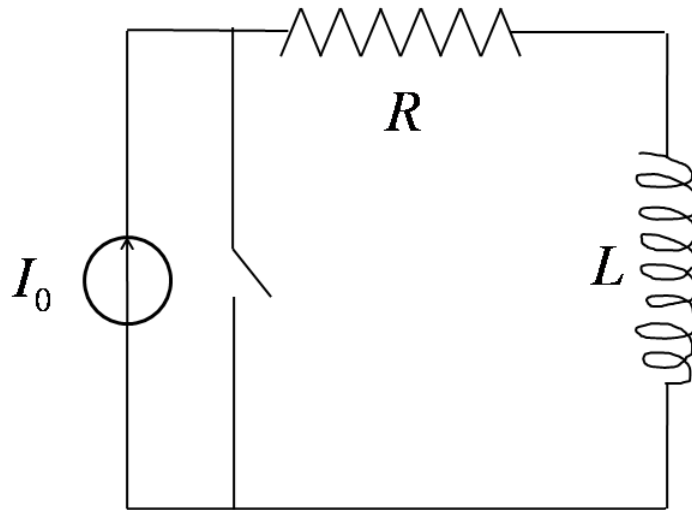


Figure 3.

Formulae

GCS units

1. $\oint \mathbf{E} \cdot d\mathbf{a} = 4\pi Q_{enc}$ $\nabla \cdot \mathbf{E} = 4\pi\rho$
2. $\oint \mathbf{B} \cdot d\mathbf{s} = \frac{4\pi}{c} I_{enc}$ $\nabla \times \mathbf{B} = \frac{4\pi}{c} \mathbf{J}$
3. $\varepsilon = -\frac{1}{c} \frac{d\phi}{dt}$ where $\phi = \int \mathbf{B} \cdot d\mathbf{a}$ $\nabla \times \mathbf{E} = -\frac{1}{c} \frac{\partial \mathbf{B}}{\partial t}$
4. $\nabla \cdot \mathbf{B} = 0$

MKS units

5. $\oint \mathbf{E} \cdot d\mathbf{a} = \frac{1}{\varepsilon_0} Q_{enc}$ $\nabla \cdot \mathbf{E} = \rho / \varepsilon_0$
6. $\oint \mathbf{B} \cdot d\mathbf{s} = \mu_0 I_{enc}$ $\nabla \times \mathbf{B} = \mu_0 \mathbf{J}$
7. $\varepsilon = -\frac{d\phi}{dt}$ where $\phi = \int \mathbf{B} \cdot d\mathbf{a}$ $\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t}$
8. $\nabla \cdot \mathbf{B} = 0$

CGS & MKS units

9. $I = \int \mathbf{J} \cdot d\mathbf{a}$
10. $V_A - V_B = \int_A^B \mathbf{E} \cdot d\mathbf{s}$
11. $V = L \frac{dI}{dt}$
12. $\varepsilon_{21} = -M_{21} \frac{dI_1}{dt}$
13. $M_{21} = M_{12}$
14. $Q = CV$
15. $I = \frac{dQ}{dt}$
16. $V = RI$
17. $P = IV$